

A blender draws 0.25 A when connected to a 120 V outlet.

- a) What is the resistance of the blender?
- b) How much power does it use?
- c) How many electrons pass through the blender in 15 s?

$$a) \quad V = IR \quad R = \frac{V}{I} = \frac{120V}{0.25A} = 480\Omega$$

$$b) \quad P = IV = (0.25A)(120V) = 30W$$

$$c) \quad I = \frac{q}{t} \quad q = I \cdot t = (0.25A)(15s) = 3.75C$$

$$1e^- = 1.6 \times 10^{-19}C$$

$$3.75C \times \frac{1e^-}{1.6 \times 10^{-19}C} = 2.34 \times 10^{19}e^-$$