

A 60 W light bulb is connected to a 120 V power supply.

- a.) How much current flows through it?
- b.) What is the resistance of the bulb?
- c.) How many electrons flow through it in 1 hour?

$$a) P = IV \quad I = \frac{P}{V} = \frac{60W}{120V} = 0.50A$$

$$b) V = IR \quad R = \frac{V}{I} = \frac{120V}{0.50A} = 240\Omega$$

$$c) I = \frac{q}{t} \quad q = I \cdot t = (0.50A) \left(1h \cdot \frac{60min}{h} \cdot \frac{60s}{min} \right) \\ = 1800C$$

$$1800C \times \frac{1e^-}{1.6 \times 10^{-19}C} = 1.1 \times 10^{22} e^-$$