

## Quiz 6a

Note Title

29/05/2011

A blender requires 210 W while working at full speed in order to frappe a smoothie. The blender motor has a resistance of 90 $\Omega$ .

If the blender draws from a 120V power source,

- a. How much current does it initially draw when the motor is turned on?
- b. How much back EMF is generated when the motor is running at full speed?

A blender requires 210 W while working at full speed in order to frappe a smoothie. The blender motor has a resistance of 40Ω.

If the blender draws from a 120V power source,

- How much current does it initially draw when the motor is turned on?
- How much back EMF is generated when the motor is running at full speed?

a.)  $V_{\text{Back}} = 0 \quad \therefore \quad E = Ir$  ✓  $I = \frac{E}{r} = \frac{120V}{40\Omega} = 3A$  ✓

b.)  $P = I^2r$   $I = \sqrt{\frac{P}{r}} = \sqrt{\frac{210}{40}} = 2.29A$

$$\begin{aligned} V_{\text{Back}} &= E - Ir \\ &= 120V - (2.29A)(40\Omega) \\ &= 28V \end{aligned}$$